

WEEKLY TEST RANKER'S BATCH TEST - 19 RAJPUR
SOLUTION Date 09-02-2020

[PHYSICS]

1. B
2. C

3. $C = \frac{\epsilon_0 A}{d}$, $C_1 = \frac{\epsilon_0 A}{2d}$ and $C_2 = \frac{K\epsilon_0 A}{2d}$

$$C_{\text{eff.}} = \frac{\epsilon_0 A}{2d} + \frac{K\epsilon_0 A}{2d} = \frac{\epsilon_0 A}{2d} (K + 1) = \frac{C}{2} (K + 1)$$

4. The given combination is equivalent to two capacitors in parallel each with plate area $A/2$ and separation d .

Then, $C_1 = \frac{K_1 \epsilon_0 (A/2)}{d} = \frac{K_1 \epsilon_0 A}{2d}$

$$C_2 = \frac{K_2 \epsilon_0 (A/2)}{d} = \frac{K_2 \epsilon_0 A}{2d}$$

5. 5 capacitors in parallel give $5 \times 2 \mu\text{F} = 10 \mu\text{F}$ capacitor. Further, two capacitors in series give a capacity $1 \mu\text{F}$. When the two combinations are connected in series, they give a resultant capacitance

$$\frac{10 \times 1}{10 + 1} = \frac{10}{11} \mu\text{F}$$

6. $C = 10 = \frac{\epsilon_0 A}{d}$

$$C' = K_1 \frac{(\epsilon_0 A/2)}{d} + K_2 \frac{(\epsilon_0 A/2)}{d}$$

$$= 2 \left(\frac{\epsilon_0 A}{2d} \right) + 4 \left(\frac{\epsilon_0 A}{2d} \right)$$

$$= 3 \left(\frac{\epsilon_0 A}{d} \right) = 3 \times 10 = 30 \mu\text{F}$$

7. $V_A - V_0 = \frac{q}{C_1}$ or $q = (V_A - V_0)C_1$

$$V_B - V_0 = \frac{q_1}{C_2} \text{ or } q_1 = (V_B - V_0)C_2$$

8. Net electric flux emitted from a spherical surface of radius a is :

$$\phi_{\text{net}} = \frac{q_{\text{in}}}{\epsilon_0} \quad [\text{According to Gauss's law}]$$

or $ES = (Aa)(4\pi a^2) = \frac{q_{\text{in}}}{\epsilon_0}$, hence $q_{\text{in}} = 4\pi \epsilon_0 Aa^3$

9. B

10. Potential at the centre of square

$$V = \frac{1}{4\pi\epsilon_0} \left[\frac{Q}{R} - \frac{q}{R} + \frac{2q}{R} + \frac{2Q}{R} \right] = 0$$

Hence, $Q = -q$

11. B

12. When the two condensers are connected in series,

$$C = \frac{2 \times 1}{2 + 1} = \frac{2}{3} \mu\text{F} \text{ and } Q = \frac{2E}{3}$$

The potential of condenser C_1 is given by:

$$V_1 = \frac{Q}{C_1} = \frac{2E}{3} < 6 \text{ kV}$$

$$\therefore E < 6 \times \frac{3}{2} < 9 \text{ kV}$$

13. C_1, C_2 and C_3 are in series:

$$\frac{1}{C'} = \frac{1}{C} + \frac{1}{2C} + \frac{1}{3C}$$

or $\frac{1}{C'} = \frac{6 + 3 + 2}{6C} = \frac{11}{6C}$

$$\therefore C' = 6C/11$$

Charge on each of the three capacitors in series is:

$$Q' = 6CV/11$$

Also charge on capacitor $C_4 = 4CV$

$$\therefore \text{Ratio} = \frac{Q'}{Q} = \frac{6CV}{11 \times 4CV} = \frac{3}{22}$$

14. When plates of capacitor are separated by a dielectric medium of dielectric constant K , its capacity,

$$C_m = \frac{K\epsilon_0 A}{d} = KC_0$$

Here, $C_0 = C$

$$\therefore C_m = KC$$

Now, two capacitor of capacities KC and C are in series, their effective capacitance,

$$\frac{1}{C'} = \frac{1}{KC} + \frac{1}{C}$$

15. Common potential = $\frac{\text{total charge}}{\text{total capacity}}$


$$\therefore V = \frac{Q}{C_1 + C_2}$$

$$\text{charge on } C_1 = C_1 V = \frac{C_1 Q}{C_1 + C_2}$$

$$\text{charge on } C_2 = C_2 V = \frac{C_2 Q}{C_1 + C_2}$$

$$\therefore \frac{\text{charge on } C_1}{\text{charge on } C_2} = \frac{C_1 V}{C_2 V} = \frac{C_1}{C_2}$$

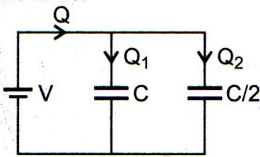16. As the capacitors are connected in parallel, therefore, potential difference across both the condensers remains the same.



$$\therefore Q_1 = CV ; Q_2 = \frac{C}{2} V$$

$$\begin{aligned} \text{Also, } Q &= Q_1 + Q_2 \\ &= CV + \frac{C}{2} V = \frac{3}{2} CV \end{aligned}$$

Work done in charging fully both the condensers is given by:

$$W = \frac{1}{2} QV = \frac{1}{2} \times \left(\frac{3}{2} CV \right) V = \frac{3}{4} CV^2$$


17. Three capacitors of capacitance C each are in series.

$$\therefore \text{Total capacitance, } C_{\text{total}} = \frac{C}{3}$$

The charge is the same (= Q), when capacitors are in series,

$$V_{\text{total}} = \frac{Q}{C_{\text{total}}} = \frac{Q}{C/3} = 3V$$

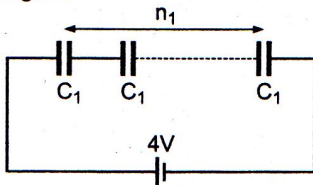18. A series combination of n_1 capacitors each of capacitance C_1 are connected to 4V source as shown in the figure.



Total capacitance of the series combination of the capacitors is,


$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_1} + \frac{1}{C_1} + \dots \text{ upto } n_1 \text{ terms} = \frac{n_1}{C_1}$$

$$\text{or } C_s = \frac{C_1}{n_1} \quad \dots(i)$$

Total energy stored in a series combination of the capacitors is,

$$\begin{aligned} U_s &= \frac{1}{2} C_s (4V)^2 \\ &= \frac{1}{2} \left(\frac{C_1}{n_1} \right) (4V)^2 \quad \dots(ii) \text{ [Using eqn. (i)]} \end{aligned}$$

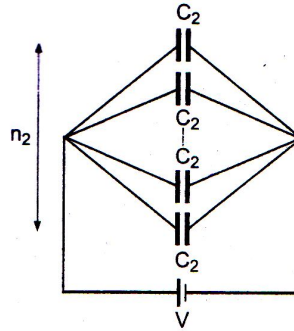A parallel combination of n_2 capacitors each of capacitance C_2 are connected to V source as shown in the figure.



Total capacitance of the parallel combination of capacitors is,

$$\begin{aligned} C_p &= C_2 + C_2 + \dots \text{ upto } n_2 \text{ terms} = n_2 C_2 \\ \text{or } C_p &= n_2 C_2 \quad \dots(iii) \end{aligned}$$

Total energy stored in a parallel combination of capacitors is,

$$U_p = \frac{1}{2} C_p (V)^2 = \frac{1}{2} (n_2 C_2) (V)^2 \quad \dots(iv)$$

[Using eqn. (iii)]

According to the given problem, $U_s = U_p$


Substituting the values of U_s and U_p from equations (ii) and (iv), we get

$$\frac{1}{2} \cdot \frac{C_1}{n_1} (4V)^2 = \frac{1}{2} (n_2 C_2) (V)^2$$

$$\text{or } \frac{C_1 \cdot 16}{n_1} = n_2 C_2$$

$$\text{or } C_2 = \frac{16C_1}{n_1 n_2}$$

19.

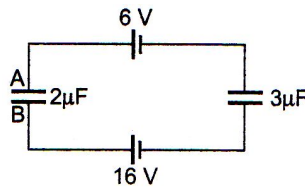


Here, $2\mu\text{F}$ and $3\mu\text{F}$ capacitors are connected in series. Their equivalent capacitance is,

$$\frac{1}{C_s} = \frac{1}{2} + \frac{1}{3} \quad \text{or } C_s = \frac{6}{5} \mu\text{F}$$

Net voltage, $V = 16\text{V} - 6\text{V} = 10\text{V}$

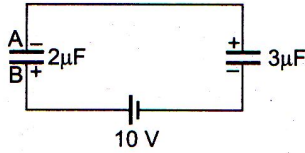The equivalent circuit diagram as shown in below figure.



Charge on each capacitor,

$$q = C_s V = \frac{6}{5} \times 10 = 12 \mu\text{C}$$

The potential difference between A and B is :

$$= -\frac{12 \mu\text{C}}{2 \mu\text{F}} = -6 \text{ V}$$

20. Electric field between the plates of a charged capacitor is given by

$$E = \frac{q}{K\epsilon_0 A}$$

where q = Charge on the plates of capacitor
 ϵ_0 = Permittivity of free space
 A = Area of the plates
 K = Dielectric constant of the medium between the plates.

It is clear from the expression that electric field inside a capacitor remains constant if medium remains same, i.e., it does not vary with distance. If medium changes than K changes. As a result of this, E decreases with increase in K but decreased value again remain same in the charged medium. Hence, in the given problem, E remains constant at a higher value in the medium of air, but in the medium of slabs E decreases As $K_2 > K_1$, so decrease in value of E in medium of K_2 is more than that found in medium of K_1 . So correct option is (c).

21.
$$U_i = \frac{1}{2} CV^2 = \frac{Q^2}{2C} \quad (\because Q = CV)$$

and
$$U_f = \frac{Q^2}{2C'} = \frac{Q^2}{2KC} = \frac{C^2 V^2}{2KC} = \frac{U_i}{K}$$

$$\Delta U = U_f - U_i = \frac{1}{2} CV^2 \left[\frac{1}{K} - 1 \right]$$

As the capacitor is isolated, so charge will remain conserved. Further, pot. diff. = $\frac{Q}{C'} = \frac{Q}{KC} = \frac{V}{K}$.

22. Initial energy stored = $\frac{1}{2} (2\mu\text{F}) \times V^2$

Energy dissipated on connection across $8\mu\text{F}$

$$= \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} V^2 = \frac{1}{2} \times \frac{2\mu\text{F} \times 8\mu\text{F}}{10\mu\text{F}} \times V^2$$

$$= \frac{1}{2} \times (1.6 \mu\text{F}) V^2$$

\therefore % loss of energy = $\frac{1.6}{2} \times 100 = 80 \%$

23. Energy, $E_1 = \frac{1}{2} C_1 V_1^2 = \frac{1}{2} \times 1 \times 10^{-6} \times (30)^2$
 $= 450 \times 10^{-6} \text{ J}$

Common potential,


$$V = \frac{q_1 + q_2}{C_1 + C_2} = \frac{1 \times 30 + 0}{1 + 2} = 10 \text{ volt}$$

$$E_2 = \frac{1}{2} (C_1 + C_2) V^2 = \frac{1}{2} (1 + 2) \times 10^{-6} \times (10)^2$$

$$= 15 \times 100 \times 10^{-6} = 150 \times 10^{-6} \text{ J}$$

Loss of energy = $E_2 - E_1 = 300 \mu\text{J}$

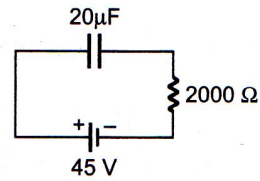24. We know that in steady state the capacitor behaves like as open circuit, i.e., capacitor will not pass the current.



So, the potential difference across the capacitor = 45 V

Hence, the final charge on the capacitor is,

$$q = CV \quad [\text{Here, } C = 20 \mu\text{F, } V = 45 \text{ V}]$$

or $q = 20 \times 10^{-6} \times 45$

or $q = 900 \times 10^{-6}$

or $q = 9 \times 10^{-4} \text{ C}$

25. Capacitance of a parallel plate capacitor is,

$$C = \frac{\epsilon_0 A}{d} \quad \dots(i)$$

where A is the area of a plate and d is the distance between them.

Energy stored in a capacitor is,

$$U = \frac{1}{2} CV^2$$

Energy stored per unit volume of a capacitor is,

$$u_E = \frac{U}{\text{Volume}} = \frac{\frac{1}{2} CV^2}{Ad}$$

$$= \frac{1}{2} \left[\frac{\epsilon_0 A}{d} \right] \frac{V^2}{Ad} \quad [\text{Using eqn. (i)}]$$

$$= \frac{1}{2} \epsilon_0 \left(\frac{V}{d} \right)^2$$

26. Flux = $\frac{q_m}{\epsilon_0}$

The two plates of the capacitor has equal and opposite charges. Hence, net charge enclosed by the given surface = 0

\therefore Flux is zero in both the cases. Hence, change in flux = 0

27. Let C be the capacitance of each capacitor.
 Then, $6 = C/5$ or $C = 30 \mu\text{F}$
 If these are connected in parallel, then equivalent capacitance will be maximum.
 $C' = 30 \times 5 = 150 \mu\text{F}$

28. Given; Capacitance of big drop (C_1) = $1 \mu\text{F}$
 Radius of small drop = r
 Number of small drops (n) = 8
 Since, volume of big drop remains the same after it is broken into eight small drops, therefore
 $\frac{4}{3} \pi R^3 = 8 \times \frac{4}{3} \pi r^3$ or $R = 2r$,

where R = radius of big drop.
 We also know that capacitance of the spherical drop (C) = $4\pi\epsilon_0 r$


i.e., $C \propto r$
 Therefore, $\frac{C_1}{C_2} = \frac{R}{r} = \frac{2r}{r} = 2$

or $C_2 = \frac{C_1}{2} = \frac{1}{2} \mu\text{F}$

Where C_2 = capacitance of each small drop.

29. Both the capacitors are in series. Therefore, charge stored on them will be same.
 Net capacity = $\frac{C(2C)}{C+2C} = \frac{2}{3} C$
 $= \frac{2}{3} \times 6 \mu\text{F} = 4 \mu\text{F}$
 Potential difference = 10 V
 $\therefore q = CV = 40 \mu\text{C}$

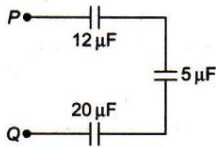30. In circuit, condenser of capacity $2 \mu\text{F}$ and $3 \mu\text{F}$ are in parallel. Their resultant capacity is $5 \mu\text{F}$.




Now, capacitor $12 \mu\text{F}$, $5 \mu\text{F}$ and $20 \mu\text{F}$ are in series. So, their resultant capacity

$$\frac{1}{C} = \frac{1}{5} + \frac{1}{20} + \frac{1}{12} = \frac{1}{3}$$

$\therefore C = 3 \mu\text{F}$

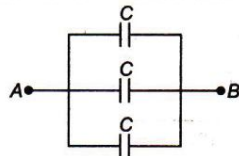- 31.

Three capacitors are in parallel. So, their equivalent capacity




$$C_p = C + C + C = 3C$$

32. Given plates are equivalent to 3 identical capacitors in parallel combination. Hence, equivalent capacitance

$$C_p = C + C + C = 3C = 3 \frac{\epsilon_0 A}{d}$$

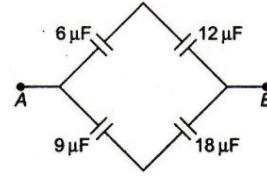33. Given circuit is balanced Wheatstone bridge circuit.





Now capacitor of capacity $6 \mu\text{F}$, $12 \mu\text{F}$ are in series and $9 \mu\text{F}$, $18 \mu\text{F}$ are also in series.

\therefore Equivalent capacitance between A and B is

$$C_{AB} = 4 + 6 = 10 \mu\text{F}$$

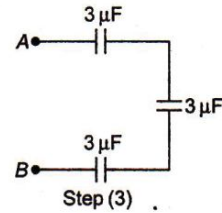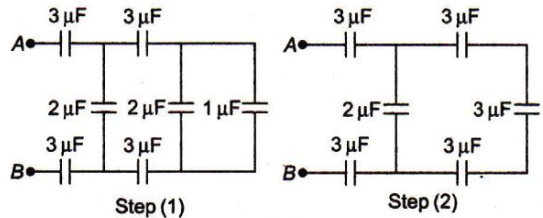
34. The given circuit can be reduced in following manner



\therefore Resultant capacity between A and B

i.e., $C_{AB} = 1 \mu\text{F}$

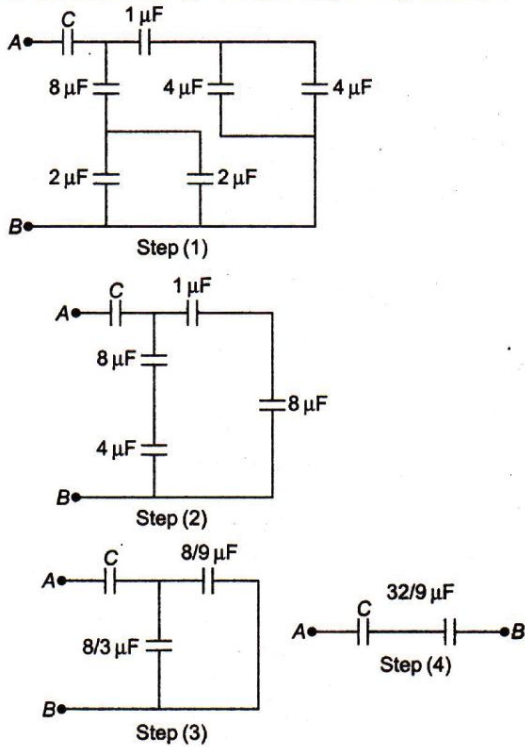
35. Given circuit can be reduced in following manner :



So, equivalent capacitance between A and B


$$C_{eq.} = 1 = \frac{\frac{32}{9} \times C}{\frac{32}{9} + C} \therefore C = \frac{32}{23} \mu F$$

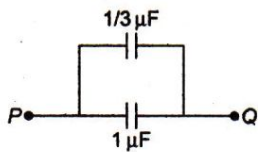36. Given circuit can be simplified as shown




$$\therefore C_{PQ} = \frac{1}{3} + 1 = \frac{4}{3} \mu F$$

37. The circuit can be redrawn as

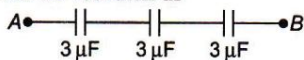


So, $C_{AB} = \frac{3}{3} = 1 \mu F$

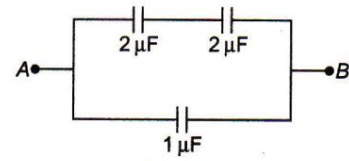38. Given circuit can be redrawn as follows.



Step (1)

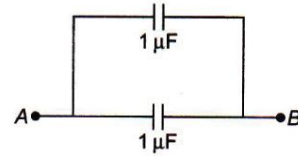


Step (2)


So, equivalent capacitance between A and B

$$C_{AB} = 1 + 1 = 2 \mu F$$

39. Given circuit can be redrawn as

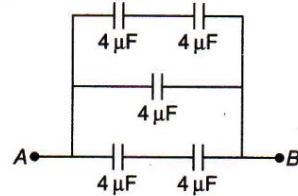

Step (1)

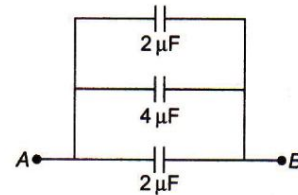

Step (2)

So, equivalent capacitance between A and B,

$$C_{AB} = 2 + 4 + 2 = 8 \mu F$$

40. Capacitors C_1 and C_2 are in series with C_3 in parallel with them.

Now,

$$C_1 = \frac{K_1 \epsilon_0 (A/2)}{(d/2)} = \frac{K_1 \epsilon_0 A}{d}$$

$$C_2 = \frac{K_2 \epsilon_0 (A/2)}{(d/2)} = \frac{K_2 \epsilon_0 A}{d}$$

and

$$C_3 = \frac{K_3 \epsilon_0 A}{2d}$$


$$C_{equivalent} = C_3 + \frac{C_1 C_2}{C_1 + C_2}$$

$$= \frac{K_3 \epsilon_0 A}{2d} + \frac{\left(\frac{K_1 \epsilon_0 A}{d}\right) \left(\frac{K_2 \epsilon_0 A}{d}\right)}{\frac{K_1 \epsilon_0 A}{d} + \frac{K_2 \epsilon_0 A}{d}}$$

$$= \frac{\epsilon_0 A}{d} \left(\frac{K_3}{2} + \frac{K_1 K_2}{K_1 + K_2} \right)$$

So, none option is correct.

41. The circuit can be redrawn as

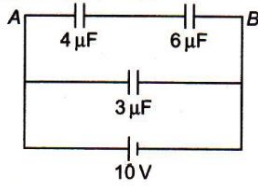


Here $4\ \mu\text{F}$ and $6\ \mu\text{F}$ are in series. So, charge is same on both. Now equivalent capacity between A and B

$$C_{AB} = \frac{6 \times 4}{6 + 4} = 2.4\ \mu\text{F}$$

So, charge on $4\ \mu\text{F}$ capacitor

$$\begin{aligned} Q &= C_{AB} \times 10 \\ &= 2.4 \times 10 \\ &= 24\ \mu\text{C} \end{aligned}$$

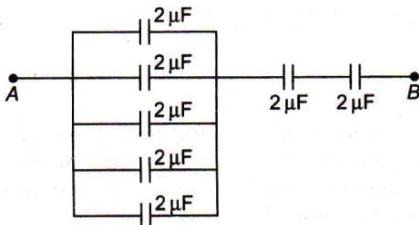42. From concept of series and parallel combination, we can easily find that in option (a) the resultant capacity is
- $\frac{10}{11}\ \mu\text{F}$
- .



The circuit can be redrawn as



$$\therefore C_{\text{eq}} = \frac{10}{10 + 1} = \frac{10}{11}\ \mu\text{F}$$

- 43.
- $q_{\text{in}} = 0$


$$\therefore \frac{Kq'}{r} + \frac{Kq}{3r} = 0 \quad (q' \rightarrow \text{on inner shell})$$

or

$$q' = -\frac{q}{3}$$

$\therefore +\frac{q}{3}$ charge will flow from inner shell to outer shell.

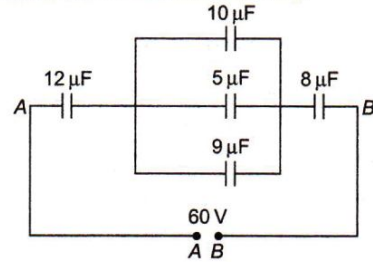44. Given circuit can be redrawn as follows.



Equivalent capacitance of the circuit

$$C_{AB} = \frac{24}{2 + 1 + 3} = 4\ \mu\text{F}$$


Total charge given by battery

$$q = C_{AB} \cdot V = 4 \times 60 = 240\ \mu\text{C}$$

Charge on $5\ \mu\text{F}$ capacitor

$$q_2 = \left(\frac{5}{10 + 5 + 9} \right) \times 240 = 50\ \mu\text{C}$$

45. Here circuit can be redrawn as.

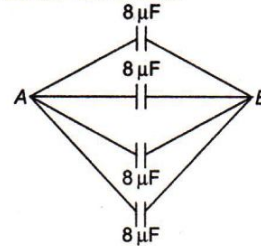

Equivalent capacitance of these capacitors

$$C_{\text{eq}} = 8 + 8 + 8 + 8 = 32\ \mu\text{F}$$

[CHEMISTRY]

53. (a)
- $n = 4 \therefore \text{Fe}^{2+}$

$$\text{If } BM = \sqrt{24} = \sqrt{4(4+2)}$$


number of unpaired e = 4

Then Fe must have +2 charge

57. (d)
- Ni^{2+}
- and
- Ti^{3+}
- ions are coloured in aqueous solution because they contain unpaired electrons.


58. (b)
- ${}_{30}\text{Zn} [\text{Ar}]^{18} 3d^{10}$
- , so
- $n = 0$
- ;
- $\text{Fe}^{2+} [\text{Ar}]^{18} 3d^6$
- , so
- $n = 4$
- ;
- $\text{Ni}^{2+} [\text{Ar}]^{18} 3d^8$
- , so
- $n = 2$
- ;
- $\text{Cu}^{2+} [\text{Ar}]^{18} 3d^9$
- , so
- $n = 1$
- .

72. (d) Cuprous ion (
- Cu^+
-)
- $3d^{10}$
- Completely filled
- d
- subshell

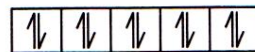 $3d^{10}$


No. unpaired $d - e^{-1}$

Cupric ion Cu^{+2}

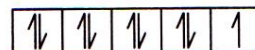 $3d^9$


1. unpaired $d - e^{-1}$

73. (c) The ability of
- d
- block element to form is due to the small and highly charged ions and vacant low energy orbital to accept lone pair electrons from ligands