

**WEEKLY TEST RANKER'S BATCH TEST - 16 RAJPUR**  
**SOLUTION Date 12-01-2020**

**[PHYSICS]**

1. Mutual inductance between two coils

$$M = - \frac{e_2}{(di_1 / dt)} = - \frac{e_1}{(di_2 / dt)}$$

Also,

$$e_1 = -L_1 \frac{di_1}{dt}$$

$$e_2 = -L_2 \frac{di_2}{dt}$$

$$\therefore M^2 = \frac{e_1 e_2}{\left(\frac{di_1}{dt}\right) \left(\frac{di_2}{dt}\right)} = L_1 L_2$$

$$\Rightarrow M = \sqrt{L_1 L_2}$$

2. Equivalent inductance

$$\frac{1}{L_{eq}} = \frac{1}{L} + \frac{1}{L}$$

$$\therefore L_{eq} = \frac{L}{2}$$

3. Self-inductance of solenoid is given by

$$\frac{\mu_0 N^2 A}{L}$$

4. Self-inductance of coil is directly proportional to square of number of turns in the coil, i.e.,

$$L \propto N^2$$

$$\therefore \frac{L_1}{L_2} = \frac{N_1^2}{N_2^2}$$

$$\therefore \frac{L}{L_2} = \frac{N^2}{(4N)^2}$$

$$\therefore L_2 = 16L$$

5. In the given circuit, three inductances are in parallel, their equivalent inductance,

$$\frac{1}{L_{eq}} = \frac{1}{3} + \frac{1}{3} + \frac{1}{3} \text{ or } L_{eq} = \frac{3}{3} = 1\text{H}$$

6. Mutual inductance between two coils depends on their degree of flux linkage, i.e., the fraction of flux linked with one coil which is when some current passes through the other coil. In figure (A) two coils with their planes are parallel. In this situation, maximum flux passes.

$$7. \quad L = \left| \frac{e}{di/dt} \right| = \frac{8}{(2/0.5)} = 2 \text{ H}$$

$$8. \quad L_p = \frac{L_1 L_2}{L_1 + L_2} \text{ and } L_s = L_1 + L_2$$

$$9. \quad M = \frac{\Delta\phi_2}{\Delta i_1} \text{ because } \phi_2 = M i_1$$

$$\therefore \Delta\phi_2 = M(\Delta i_1)$$

$$10. \quad e_2 = M \left( \frac{di_1}{dt} \right) = i_2 R_2$$

$$\therefore \left( \frac{di_1}{dt} \right) = \frac{i_2 R_2}{M} = \frac{(0.4)(5)}{0.5} = 4 \text{ A/s}$$

12. Growth of current in the circuit is given by

$$i = i_0(1 - e^{-Rt/L})$$

where,  $i_0$  is peak value of current and

$$i_0 = \frac{5}{5} = 1 \text{ A}$$

$$\therefore i = 1(1 - e^{-5 \times 2/10}) \\ = (1 - e^{-1}) \text{ A}$$

13. In case of growth of current in a  $L$ - $R$  circuit, the current in the circuit grows exponentially with time 0 to the maximum value  $i_0 = E/R$ .

14. In one time constant current reduces to  $\frac{1}{e}$  times.

15. Current in the circuit  $i = V/R = 10/2 = 5 \text{ A}$

$\therefore$  Magnetic energy stored in the coil

$$U = \frac{1}{2} Li^2 \\ = \frac{1}{2} \times 2 \times (5)^2 \\ = 25 \text{ J}$$

16. During growth of current in the coil

$$i = i_0(1 - e^{-Rt/L})$$

For  $i = \frac{i_0}{2}$

$$\frac{i_0}{2} = i_0(1 - e^{-Rt/L})$$

$$\therefore t = 0.693 \frac{L}{R} \\ = 0.693 \times \frac{300 \times 10^{-3}}{2} = 0.1 \text{ s}$$

17. Growth of current in the circuit is

$$i = i_0(1 - e^{-Rt/L})$$

$$\Rightarrow \frac{di}{dt} = \frac{d}{dt} i_0 - \frac{d}{dt} i_0 e^{-Rt/L}$$

$$\therefore \frac{di}{dt} = 0 - i_0 \left( -\frac{R}{L} \right) e^{-Rt/L} = \frac{i_0 R}{L} e^{-Rt/L}$$

Initially,  $t = 0$ ,

$$\therefore \frac{di}{dt} = \frac{i_0 R}{L} = \frac{E}{L} = \frac{5}{2} = 2.5 \text{ A/s}$$



$$18. E = \frac{1}{2} Li^2$$

19.

20.

$$21. P = F \cdot v = F m \cdot v \\ = i l B \cdot v \\ = \left( \frac{B v l}{R} \right) \cdot l B \cdot v \\ = \frac{B^2 l^2 v^2}{R}$$

$$22. V_a - i R - L \frac{di}{dt} = V_b$$

$$\therefore V_a - V_b = i R + L \frac{di}{dt}$$

According to given conditions :

$$8 = 2R + L \quad \dots(i)$$

$$4 = 2R - L$$

Solving these two equations we get,

$$R = 3 \Omega \text{ and } L = 2 \text{ H}$$

$$23. V = L \frac{di}{dt} \text{ or } V \propto L \quad \left( \text{as } \frac{di}{dt} \rightarrow \text{same} \right)$$

$$\therefore \frac{V_1}{V_2} = \frac{L_1}{L_2} = 4$$

$$P = Vi = \text{constant}$$

$$\therefore i \propto \frac{1}{V}$$

$$\text{or } \frac{i_1}{i_2} = \frac{V_2}{V_1} = \frac{1}{4}$$

$$W = \frac{1}{2} Li^2$$

$$\therefore \frac{W_1}{W_2} = \frac{L_1}{L_2} \left( \frac{i_1}{i_2} \right)^2 \\ = (4) \left( \frac{1}{16} \right) = \frac{1}{4}$$

$$24. \tau_L = \frac{L}{R} = \frac{1}{2} \text{ second}$$

$$i = i_0 (1 - e^{-t/\tau_L})$$

$$\therefore \frac{i_0}{i} = \frac{1}{1 - e^{-t/\tau_L}}$$

Substituting,  $t = 1$  second and  $\tau_L = \frac{1}{2}$  s

$$\text{We get, } \frac{i_0}{i} = \frac{e^2}{e^2 - 1}$$

25. For a capacitor,

$$i = \left( \frac{dq}{dt} \right) = C \cdot \left( \frac{dV}{dt} \right), \text{ i.e., } i = \text{constant if } \frac{dV}{dt} = \text{constant}$$

$$\therefore C = \frac{i}{\left( \frac{dV}{dt} \right)} = \frac{1}{2} = 0.5 \text{ F}$$

26.  $V = 2t$

$\therefore L \cdot \frac{di}{dt} = 2t$

or  $2 \cdot \frac{di}{dt} = 2t$

or  $\frac{di}{dt} = t$

or  $(di) = t (dt)$

Integrating, we get

$$i = \frac{t^2}{2}$$

i.e.  $i-t$  graph is a parabola.

At  $t = 2$  s,  $i = 2$  A

$\therefore U = \frac{1}{2} Li^2 = \frac{1}{2} \times 2 \times 4 = 4$  J

$$\frac{dU}{dt} = Li \left( \frac{di}{dt} \right)$$

$$= (2) \left( \frac{t^2}{2} \right) (t) = t^3$$

At  $t = 1$  second,  $\frac{dU}{dt} = 1$  J/s

27.

$$E l = \frac{d\phi}{dt}$$

or  $E (2\pi R) = \pi R^2 \cdot \frac{dB}{dt} = \pi R^2 (8t)$

$\therefore E = 4Rt$

$$F = qE = 4qRt$$

(tangential)

$$\tau_f = 4qR^2 t$$

$$\tau_r = (\mu mgR)$$

When  $\tau_f > \tau_r$ , ring will start rotating.

At 2 sec,

$$8qR^3 = \mu mgR$$


$\therefore \mu = \frac{8qR}{mg}$

28. Since you are decreasing current in the circuit by increasing resistance of the circuit.

Induced emf across inductor will support 20 V battery.

Hence, net emf of the circuit is greater than 20 V. Or current in the circuit is more than 4 A.

29. After short circuiting the battery.

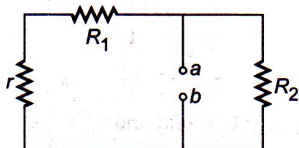

$$R_{ab} = \frac{R_2 (R_1 + r)}{R_2 + R_1 + r}$$

$\therefore \tau_L = \frac{L}{R_{net}} = \frac{L (R_1 + R_2 + r)}{(R_1 + r) R_2}$

30.

$$I = \frac{PD}{\text{Resistance}}$$


$$\therefore PD = 2 \times 12 = 24 \text{ V} = B v l$$

$$\text{Here } l = AD \sin 37^\circ = 0.3 \times \frac{3}{5} = 0.18 \text{ m}$$

$$\therefore v = \frac{24}{Bl} = \frac{24}{4 \times 1.08} = \frac{100}{3} \text{ m/s}$$

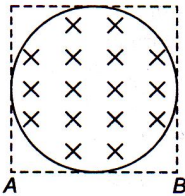31.

$$V_{ba} = \int \mathbf{E} \cdot d\mathbf{l} = \frac{1}{4} \left( \frac{d\phi}{dt} \right)$$




$$= \frac{1}{4} (\pi R^2) \cdot \frac{dB}{dt} = \frac{\pi R^2 \alpha}{4}$$

32. Magnetic lines on circular loop, due to current in wire AB are tangential to its plane.

$$\therefore \phi = 0 \text{ or } \frac{d\phi}{dt} = 0 \text{ or induced emf} = 0.$$

33.

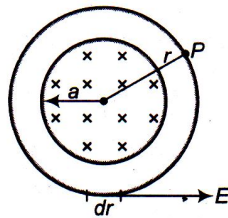

Draw a concentric circle of radius  $r$ . The induced electric field ( $E$ ) at any point on the circle is equal to that at  $P$ .  
For this circle, induced emf

$$e = \oint \mathbf{E} \cdot d\mathbf{l} = \left| \frac{d\phi}{dt} \right| = A \left| \frac{dB}{dt} \right|$$

$$\therefore E = \oint dl = \pi a^2 \left| \frac{dB}{dt} \right|$$

$$\text{(but, } \oint dl = 2\pi r)$$

$$\therefore E \times (2\pi r) = \pi a^2 \left| \frac{dB}{dt} \right|$$

$$\therefore E = \frac{a^2}{2r} \left| \frac{dB}{dt} \right|$$

$$\Rightarrow E \propto \frac{1}{r}$$

34. According to Fleming's right hand rule  $P$  is at higher potential and  $Q$  is at lower potential. Therefore,  $A$  is positively charged and  $B$  is negatively charged.


Also, charge

$$Q = CV = C(Bvl) \\ = 10 \times 10^{-6} \times 4 \times 2 \times 1 = 80 \mu\text{C}$$

$$\therefore q_A = 80 \mu\text{C}$$

$$\text{and } q_B = -80 \mu\text{C}$$

35. For rotating rod, induced emf

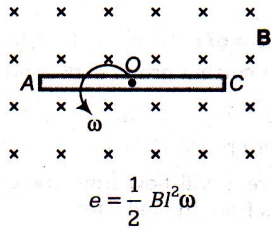


$$\text{For part } AO, \quad e_{OA} = e_O - e_A = \frac{1}{2} Bl^2 \omega$$

For part  $OC$ ,

$$e_{OC} = e_O - e_C = \frac{1}{2} B(3l)^2 \omega$$

$$\therefore e_A - e_C = 4Bl^2 \omega$$

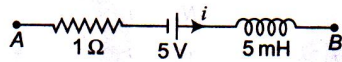36. Applying Kirchhoff's second law to above circuit,



$$V_A - iR + 15 - L \frac{di}{dt} = V_B$$

$$\text{or } V_A - 5 \times 1 + 15 - (5 \times 10^{-3})(-10^3) = V_B$$

$$\therefore V_B - V_A = 15 \text{ volt}$$

$$37. \text{ (c) } i = \frac{|e|}{R} = \frac{N}{R} \cdot \frac{\Delta B}{\Delta t} A \cos \theta$$

$$= \frac{20}{100} \times 1000 \times (25 \times 10^{-4}) \cos 0^\circ$$

$$\Rightarrow i = 0.5 \text{ A}$$

38.

$$2\pi v = 377 \Rightarrow v = 60.03 \text{ Hz}$$

39.

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}} = \frac{120}{1.414} = 84.8 \text{ V}$$

40.

$$\text{Phase difference } \Delta\phi = \phi_2 - \phi_1 = \frac{\pi}{6} - \left(\frac{-\pi}{6}\right) = \frac{\pi}{3}$$



41.

The current takes  $\frac{T}{4}$  sec to reach the peak value.

In the given question  $\frac{2\pi}{T} = 200\pi \Rightarrow T = \frac{1}{100}$  sec

$\therefore$  Time to reach the peak value =  $\frac{1}{400}$  sec

42.

$$i_{r.m.s} = \frac{6}{\sqrt{2}} = 3\sqrt{2} \text{ A}$$

43.

$$i_{r.m.s} = \frac{V_{r.m.s.}}{R} = \frac{200}{40} = 5 \text{ A} \Rightarrow i_0 = i_{r.m.s.} \sqrt{2} = 7.07 \text{ A}$$

44.

$$E = E_0 \cos \omega t = E_0 \cos \frac{2\pi t}{T}$$

$$= 10 \cos \frac{2\pi \times 50 \times 1}{600} = 10 \cos \frac{\pi}{6} = 5\sqrt{3} \text{ volt.}$$

45.

$$I = I_1 \cos \omega t + I_2 \sin \omega t$$

$$(I^2) = \text{mean} = \overline{I_1^2 \cos^2 \omega t} + \overline{I_2^2 \sin^2 \omega t}$$

$$+ 2I_1 I_2 \overline{\cos \omega t \cdot \sin \omega t}$$

$$= I_1^2 \cdot \frac{1}{2} + I_2^2 \cdot \frac{1}{2} + 2I_1 I_2 \times 0$$

$$I_{r.m.s.} = \frac{(I_1^2 + I_2^2)^{1/2}}{\sqrt{2}}$$

### [CHEMISTRY]


46. The order of acid strength is  $\text{RCOOH} > \text{HOH} > \text{ROH} > \text{HC}\equiv\text{CH}$

Electron-releasing alkyl group R in ROH makes it lesser acidic than  $\text{H}_2\text{O}$ .

47. Nearer the chlorine to the  $-\text{COOH}$  group, stronger the acidity. Hence, the correct order is




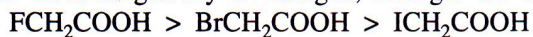48. Larger the electronegativity of halogen, stronger the acidity. Hence, the correct order is




49. Tollens reagent gives white precipitate with methanoic acid and not with ethanoic acid.

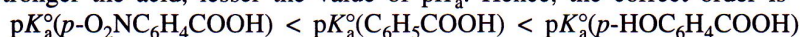
50. Electron-releasing group makes benzoic acid a weaker acid while electron-attracting group makes it a stronger acid. Stronger the acid, lesser the value of  $\text{p}K_a^\circ$ . Hence, the correct order is



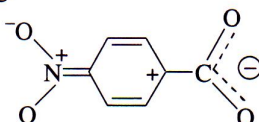51. The nitro group interacts with the phenyl ring and thereby induces some positive charge on the ring bearing the  $\text{COO}^-$  causing a strong electron-withdrawing inductive effects on  $\text{COO}^-$  group. This effect is base-stabilizing and thus acid strengthening.



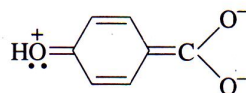52. At *para* position, —OH places negative charge on the carboxylate group and thus making it




weaker than benzoic acid. This effect predominates over its electron-withdrawing acid strengthening inductive effect. However, at *meta* position, there is no such resonance effect and only inductive effect operates and because of its nearness to the COOH group, *meta* isomer is stronger acid than its *para* isomer.

53. *Meta* hydroxy is stronger than *para* isomer (see Q.52). Because of the *ortho* effect, *ortho* isomer is the strongest acid.
54. Increasing crowding near the site of esterification decreases the rate of esterification. Hence, the correct order is  $1^\circ > 2^\circ > 3^\circ$ .
55. Same as Q 54 The correct order is  $RCH_2COOH > R_2CHCOOH > R_3CCOOH$
56.  $\alpha$ -Hydrogen is replaced by chlorine. The product is  $CH_3CH(Cl)COOH$ .
57. Heating calcium formate along with calcium benzoate produces benzaldehyde.
- 58.

The products are CO and  $H_2O$ .  $HCOOH \xrightarrow{\text{Conc. } H_2SO_4} CO + H_2O$ .

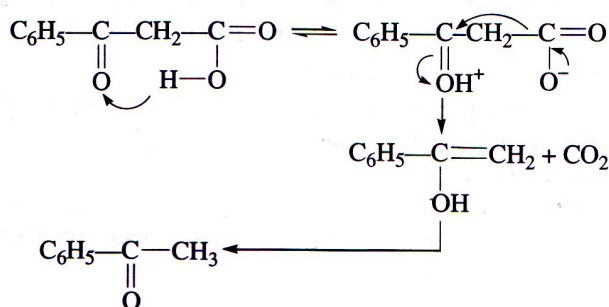59. The Hell-Volhard-Zelinsky reaction is used in the synthesis of  $\alpha$ -haloacids.
60. In *p*- $CH_3COC_6H_4COOH$ , the CO group is also reduced by  $LiAlH_4$ .
61. Succinic acid ( $HOOCH_2CH_2COOH$ ) gives cyclic anhydride on heating.
62.  $\beta$ -Ketoacids are unstable acids. These readily undergo decarboxylation through a cyclic transition state




- 63.
64. Bromine is lesser electronegative than fluorine. Bromine attached to  $\beta$ -carbon will cause least enhancement in the dissociation of halo substituted propanoic acid.
65. Carboxylic acids have relatively high boiling points because of hydrogen bonds. Their boiling points are somewhat higher than those of alcohols of comparable molar masses. Since there exists no hydrogen bondings in aldehydes, their boiling points are lower than those of corresponding alcohols.
66.  $BH_3/THF$  followed by  $H_3O^+$  reduces only —COOH group without affecting —CO— group.  $LiAlH_4$  reduces only —COOH group without affecting  $C=C$  group.
67. The order of reactivity is acid chloride  $>$  anhydride  $>$  ester.
68. The correct order is  $Cl^- < RCOO^- < RO^-$ .
69. The correct order is  $Cl^- < RO^- < NH_2^-$ .
70. Electron-withdrawal group increasing reactivity of hydrolysis while the electron-releasing group decreases reactivity. The correct order is  $p-O_2NC_6H_4COCl > PhCOCl > p-CH_3OC_6H_4COCl$ .
71. (a)
72. (a)
73. (b)
74. (b)



75. (a)

76.

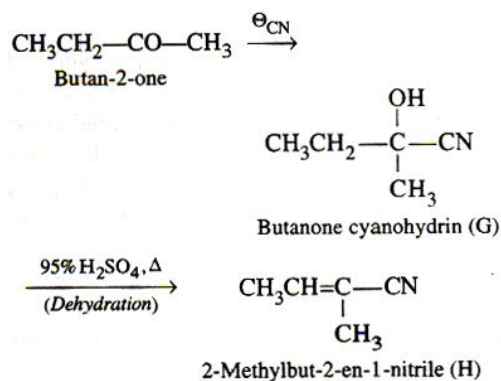

Please note that hydrolysis of cyanides to carboxylic acids requires addition of a molecule of  $\text{H}_2\text{O}$ . Since 95%  $\text{H}_2\text{SO}_4$  cannot supply  $\text{H}_2\text{O}$ , therefore, dehydration of (G) occurs to give (H).

77.

Due to ortho-effect, *o*-nitrobenzoic acid is the strongest acid. Further since electron-withdrawing groups such as  $\text{NO}_2$  increase while electron-donating groups such as  $\text{OH}$  decrease the acid strength *w.r.t.* parent acid, therefore, the overall acidity increases in the order :  $\text{C} < \text{D} < \text{B} < \text{A}$ , *i.e.*, option (d) is correct.